NOW you can clearly understand and easily design circuits --

AND, come up with the specific performance attributes you want.

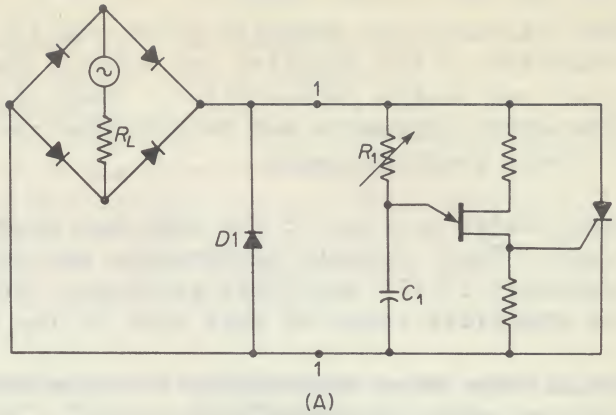

(A)

WITH A MINIMUM OF TIME AND EFFORT SPENT, YOU CAN OBTAIN A THOROUGH, WORKING KNOWLEDGE OF A WIDE RANGE OF TRANSISTOR CIRCUITS...

at home...in your spare moments...with

TRANSISTOR CIRCUIT ANALYSIS AND DESIGN

by JOHN J. CORNING

448 pp., 317 illus., 6x9" (Sept. 1965)

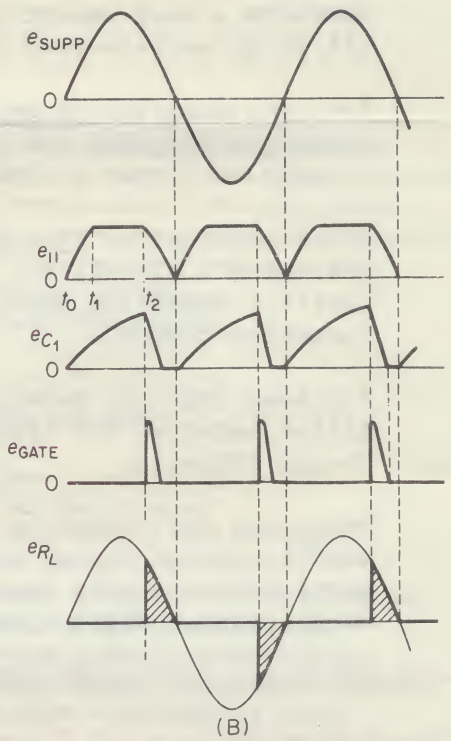

(B)

Fig. 15.27 (A) A-C phase-control circuit using a silicon-control rectifier. (B) Pertinent circuit waveforms.

NOW, you can quickly and easily learn the principles of circuit analysis. Even more important, you will see how to apply these principles to design circuits with the specific performance attributes you want.

A WEALTH OF TRANSISTOR INFORMATION CAN BE YOURS.

You get discussions of a broad scope of circuits in detail -- d-c bias techniques, a-c equivalent circuits, small and large signal amplifiers, frequency effects, high frequency amplifiers, oscillators, pulse circuits and power supplies.

You see how to utilize many semiconductor types -- unijunction transistors, tunnel diodes, rectifiers and silicon controlled rectifiers.

REMAINS TIMELY FOR YEARS...

Transistor Circuit Analysis and Design will remain useful and up-to-date for years to come. It's broad base of technical material will cope with "state of the art" semiconductor technology and circuit design requirements for many years. In treating oscillators and pulse circuits, unijunction devices and tunnel diodes are discussed extensively and supplement the conventional content of feedback oscillators and two transistor arrays. The same philosophy is maintained in treating controlled rectifiers in power control circuitry.

USEFUL SELF-STUDY AIDS...

Many illustrative examples guide you to thorough understanding of all topics and insure retention of the material you cover. These examples demonstrate the application of analytical and design philosophies. They also serve as ready reference and refresher media from which engineers and technicians can extrapolate solutions to problems they encounter in their every-day work.

Every major section of the book has examples. Each example involves real life considerations. Thus, dynamic performance and degree of d-c bias stability are considered simultaneously in all amplifier problems. This is but one of many situations which illustrate the practical value of this book to the working engineer.

Check these many outstanding features which will make this book a valuable addition to your personal, technical library:

Contains a vast amount of analytical and design data -- all in an easy-to-read and easy-to-understand style.

Presents material on R-C circuits, cascade stages, and frequency response not presented elsewhere in such breadth or with so direct a link to real-case circuit design.

Gives material on bias networks which is truly useful for designing a circuit for any given operating point with specific operating point controls in case of transistor parameter change.

Provides complete material on power supplies. Explains filter networks and regulated supplies and gives meaningful design criteria.

Discusses very complete graphical techniques as a tool for handling large signal amplifier design. These techniques supplement key math equations to any large signal amplifier requirement - Class A single ended or Class AB push-pull.

PLUS, with the aid of this book, you will be able to:

1. Understand current directions and junction phenomena in diodes and transistors.
2. Develop the ability to design circuits to achieve any desired operating point and stability.

TECHNICIANS -- Here's the easy way to acquire competence in understanding transistor circuitry. In your spare time, you can read this most complete single volume from which a thorough grasp of transistor knowledge can be obtained. What's more - you need only a background in algebra and basic electrical circuits.

ENGINEERS -- You see how to reconstruct the salient features of a broad scope of circuits designs: amplifiers, oscillators, and biasing networks. The informative, factual content and the availability of so many illustrative examples, provide a meaningful step-by-step refresher as well.

AUTHORITATIVE GUIDANCE ASSURES UNDERSTANDING...

The author, JOHN J. CORNING, is currently Manager of Monolithic Circuit Packaging Engineering at International Business Machines Corporation. Mr. Corning has developed a knack for explaining transistors, applications and design details so they come through

crystal clear. He has taught transistor courses to professional people at the General Electric Co. and has also taught at Mohawk Valley Community College, Utica, New York for five years.

But, you must see this book to appreciate it. You must at least leaf through it to see how easy it can be for you to obtain a valuable, working knowledge of transistors.

If you are not completely satisfied with the complete coverage of all phases of transistor applications and design factors, with the easy-to-read and understand style, with the many illustrative examples which insure retention of all material -- simply return the book and owe nothing. ABSOLUTELY NO OBLIGATION TO BUY.

Send the enclosed card today. Don't delay. A knowledge of transistors could mean a step up for you. Do it the easy way - send for Corning's Transistor Circuit Analysis and Design TODAY.

TABLE OF CONTENTS

1 Semiconductor materials

1.1 Review of electron theory
1.2 Conductors and insulators
1.3 Intrinsic semiconductors
1.4 N-type semiconductors
1.5 P-type semiconductors

2 Junction phenomena

2.1 The basic PN junction
2.2 Equilibrium junction currents
2.3 The reversed bias junction
2.4 The forward bias junction
2.5 The PN junction as a rectifier
2.6 Voltage breakdown
2.7 Equivalent circuit of a diode

3 Fundamentals of transistor action

3.1 Proximate independent junctions
3.2 Phenomena of interacting junctions
3.3 NPN and PNP comparisons
3.4 The transistor as an active device
3.5 Transistor connections

4 Attributes of the real transistor

4.1 Common-base leakage currents
4.2 Common-base breakdown voltage
4.3 Common-emitter leakage currents
4.4 Common-emitter breakdown voltages
4.5 Summary

5 Transistor static characteristics

5.1 Static characteristics
5.2 Common-base input characteristic
5.3 Common-base reverse-voltage characteristic
5.4 Common-base output characteristic
5.5 Common-base forward-current characteristic
5.6 Common-emitter input characteristic
5.7 Common-emitter reverse-voltage characteristic
5.8 Common-emitter output characteristic
5.9 Common-emitter forward-current characteristic
5.10 Common-collector comments
5.11 Temperature effects
5.12 Special characteristics

6 D-C bias techniques

6.1 General considerations
6.2 Fixed-bias technique
6.3 Design example: fixed-bias circuit
6.4 Current Feedback Principles
6.5 Design example: current-feedback biasing
6.6 Basic voltage feedback principle
6.7 Voltage feedback—detailed analysis
6.8 Design example: voltage-feedback biasing
6.9 Modified voltage-feedback biasing
6.10 Design example: modified voltage-feedback biasing
6.11 Combination current–voltage-feedback detailed analysis
6.12 Design example: combination current-voltage feedback biasing
6.13 Modified current-voltage feedback biasing
6.14 Design example: modified combination current-voltage feedback
6.15 Nonlinear compensation techniques

7 Transistor a-c equivalent circuits

7.1 Equivalent circuit possibilities
7.2 Developing the *h*-parameters
7.3 The *r*-equivalent circuit
7.4 *h-r* parameter interelations
7.5 *h*-parameter relations for each transistor connection
7.6 Sample of *h*-parameter calculation
7.7 Effects of operating point
7.8 Modified *h*-parameters
7.9 Example: *h*-paramenter modification by a single element
172
7.10 *h*-parameter modification due to several elements

7.11 Normalizing *h*-parameter modifications
7.12 Design example to obtain specific modified *h*'s
7.13 Summary

8 Properties of low-frequency amplifiers

8.1 General-case situation
8.2 Comparison of the possible connections
8.3 Further discussion of power gain
8.4 Example: calculating circuit performance
8.5 Circuit design using emitter by-pass capacitance

9 Low-frequency cascade amplifiers

9.1 General-case analysis procedures
9.2 Transformer coupling
9.3 *RC*-coupled circuits—iterative case
9.4 *RC*-coupled circuits—general-case analysis
9.5 Design example: *RC*-coupled amplifier
9.6 *RC*-coupled circuit using current-feedback biasing
9.7 Design example: *RC*-coupled amplifier using current-feedback bias
9.8 Cascading *RC*-coupled stages

10 Frequency effects in audio amplifiers

10.1 General-case frequency-dependent circuits
10.2 Specific analysis transistors at low frequency
10.3 Example: coupling capacitor effects on performance
10.4 Example: by-pass capacitor effects on performance
10.5 Specific analysis—transistors at high frequency
10.6 Example: transistor parameters at high frequency
10.7 Frequency response of multistage amplifier
10.8 Example: performance of multistage circuit
10.9 Basic principles of controlling frequency response
10.10 Specifics of negative-feedback circuits
10.11 Tone-control circuits—bass boost
10.12 Design example for bass-boost tone control
10.13 Tone-control circuits—treble boost
10.14 Design example: treble-boost tone control
10.15 Combined bass-treble control using feedback
10.16 Design example: combination control using feedback
10.17 Tone control with coupling circuitry
10.18 Design example: coupling-circuitry tone control
10.19 Summary

11 Low-frequency large-signal amplifiers

11.1 Large-signal amplifiers basic considerations
11.2 Transistor considerations for power-amplifier use
11.3 Direct-coupled Class A
11.4 Example: direct-coupled Class A circuit
11.5 Transformer-coupled Class A
11.6 Example: transformer-coupled Class A circuit
11.7 Class A *RC*-coupled
11.8 Disortion in Class A amplifiers
11.9 Class B push-pull amplifier theory
11.10 Class AB push-pull theory
11.11 Biasing the Class AB stage
11.12 Input considerations—Class AB circuits
11.13 Design example for Class AB
11.14 Distortion in Class AB amplifiers
11.15 Special audio circuits
11.16 Summary

12 High-frequency amplifier applications

12.1 Transistor behavior at high frequencies
12.2 General considerations—High-frequency amplifiers
12.3 Example: high-frequency performance calculations
12.4 Narrow-band amplifiers
12.5 Narrow-band design problem
12.6 Tuned-amplifier applications
12.7 Wide-band amplifiers
12.8 Review of high-frequency transistors

13 Oscillator principles and circuits

13.1 Basic-oscillator principles
13.2 Feedback oscillators
13.3 Tunnel-diode theory
13.4 Tunnel-diode sinusoidal oscillators
13.5 Example: tunnel-diode sinusoidal oscillator
13.6 Unijunction transistor theory
13.7 Unijunction transistor pelaxation oscillators
13.8 Example: unijunction pelaxation oscillator performance
13.9 Tunnel-diode pelaxation oscillator
13.10 Example: tunnel-diode relaxation oscillator
13.11 Astable multivibrators
13.12 Summary

14 Pulse circuits

14.1 Monostable multivibrators
14.2 Monostable tunnel-diode circuits
14.3 Bistable multivibrators
14.4 Counting circuits
14.5 Tunnel-diode counters
14.6 Logic-circuit fundamentals
14.7 Summary

15 Power supply and control circuits

15.1 Basic power-supply considerations
15.2 Full-wave rectifier circuit
15.3 Example: full-wave rectifier
15.4 Bridge-rectifier circuit
15.5 Capacitor input filter
15.6 Capacitor input filter example
15.7 Voltage doubler circuit
15.8 Inductor input filters
15.9 Choke input filter example
15.10 Regulated power supplies
15.11 Regulated-supply example
15.12 Controlled-rectifier theory
15.13 D-C switching application for controlled rectifier
15.14 A-C phase-control application for controlled rectifier
15.15 Summary

16 Laboratory experiments

16.1 Diode characteristics and applications
16.2 Transistor characteristics
16.3 D-C bias circuits

PRENTICE-HALL
ENGLEWOOD CLIFFS, N. J.

DEGB